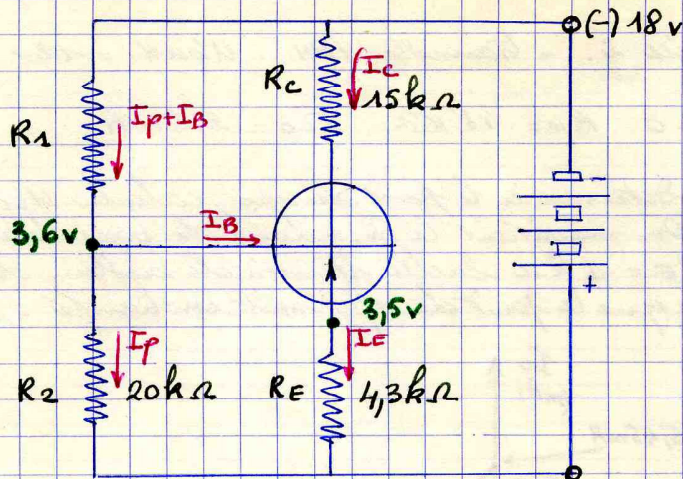


37. n° 8 page 270. n° 9. n° 10.



8. a) $I_C = 0,8 \text{ mA}$ $I_E = I_B + I_C = \underline{0,81 \text{ mA}}$
 $U_{BE} = 0,1 \text{ V}$

b) $R_E = \frac{U_{BE} - U_{CE} - U_{CE}}{I_E} = \frac{18 - 15 \times 0,8 - 2,5}{0,81}$

$R_E = \frac{3,5}{0,81} = \underline{4,3 \text{ k}\Omega}$

c) $U_{BM} = 3,5 + 0,1 = 3,6 \text{ V}$
 $I_{depon} = \frac{U_{BM}}{R_2} = \frac{3,6}{20} = 0,18 \text{ mA ou } \underline{180 \mu\text{A}}$

$(I_P \gg I_B)$

$R_1 = \frac{U_{R1}}{I_P + I_B}$ $U_{R1} = 18 - 3,6 = 14,4 \text{ V}$

$R_1 = \frac{14,4}{180 + 10} = \frac{14,4}{190} = 0,075789 \text{ k}\Omega$

$R_1 = \underline{75,789 \Omega} \# \underline{70,580 \Omega} \underline{75,800 \Omega}$

9. 270.

$\Delta I_C \uparrow \Rightarrow I_E \uparrow \Rightarrow U_{EM} \uparrow \Rightarrow U_{BE} = (U_{BM} - U_{EM}) \downarrow \Rightarrow$

$I_B \downarrow \Rightarrow \underline{I_C \downarrow}$