

maille d'entrée :

$$M_i = h_{ue} \cdot i_b + R_E \cdot i_c$$

" d'entrée : $M_o = + R_E \cdot i_c$.

$$G_u = M_o =$$

$$\frac{M_i}{i_b} = h_{21} \cdot i_b + h_{22} \cdot M_o$$

$$i_c = (\beta+2) \cdot i_b + \frac{M_o}{\beta}$$

$$i_c = (\beta+2) \cdot i_b + \frac{f}{\beta + R_E} \rightarrow |G_i| = \frac{i_c}{i_b} = \frac{f(\beta+1)}{\beta + R_E}$$

$$|G_i| = \frac{12,5 \times 122}{12,5 + 2,7} = \underline{100}$$

$$\begin{aligned} - G_u &= \frac{M_o}{M_i} = \frac{R_E \cdot i_c}{h_{21} \cdot i_b + R_E \cdot i_c} = \frac{R_E}{h_{21} + R_E} \\ &= \frac{R_E}{R_E + h_{ue} \cdot \frac{f(\beta+1)}{\beta + R_E}} = \frac{\frac{f R_E (\beta+1)}{h_{21} \cdot i_c / (\beta + R_E) + f \cdot R_E / (\beta+1)}}{f(\beta+1)} = \underline{0,993} \end{aligned}$$

Résistance d'entrée :

$$\begin{aligned} R_u &= \frac{M_i}{i_b} = \frac{h_{ue} \cdot i_b + R_E \cdot i_c}{i_b} = h_{ue} + R_E \cdot G_i \\ &= h_{ue} + \frac{R_E \cdot f(\beta+1)}{\beta + R_E} = \underline{271 \text{ k}\Omega} \end{aligned}$$